

# 1 Objective

The objective is to analyze a circuit and measure the real values to validate the calculated values [1].

# 2 Equipment Used

- Digital Multimeter
- DC Power Supply
- Resistors:  $470\Omega$ ,  $1K\Omega$  (2),  $5.1k\Omega$ ,  $10k\Omega$

# 3 Experiment Setup

# 4 Results

**Table 8-1: Resistors Values [1]**

Resistance	Measured ( $K\Omega$ )	Color Code ( $K\Omega$ )	Error (%)
$R_1$			
$R_2$			
$R_3$			
$R_4$			
$R_5$			

**Table 8-2: Mesh Currents [1]**

Current	Measured (mA)	Calculated (mA)	Error (%)
$I_A$		.813 mA	
$I_B$		-.404 mA	
$I_C$		-.913 mA	

**Table 8-3: Resistors Voltages [1]**

	Measured	Mesh Method	Nodal Analysis	Superposition	Simulation
$V_{R1}$		4.1463 V	4.43368 V	4.1466 V	
$V_{R2}$		.18988 V	-1.2158 V	-.01897 V	
$V_{R3}$		9.13 V	-8.21786 V	-9.1276 V	
$V_{R4}$		.409 V	.566316 V		
$V_{R5}$		.509 V	1.78213 V		

**Table 8-4: Resistors Current [1]**

	Measured	Mesh Method	Nodal Analysis	Superposition	Simulation
$I_{R1}$		.813 mA	.869 mA	.81305 mA	
$I_{R2}$		-.404 mA	-2.386 mA	-.04037 mA	
$I_{R3}$		-.913 mA	-8.21786 mA	-.91276 mA	
$I_{R4}$		.409 mA	.566316 mA		
$I_{R5}$		.509 mA	1.78213 mA		

# 5 Conclusion

# References

- [1] UNCC ECE Department. Network analysis, 2023. [Online; accessed 10 November 2023].